

TECHNOLOGICAL UNIVERSITY OF THE PHILIPPINES
ELECTRONICS ENGINEERING DEPARTMENT

ASSIGNMENT NO. 3

CPET11 – BET-CPET-3A / 7:00 AM – 10:00 AM W

Submitted By:

Arenas, Joseph

Estrada, Cyrusz Adrienne

Gutierrez, Geo Kentzer

Pacis, Lian Gil

Recaña, Jordan

Submitted To:

Prof. Ralph Sherwin Corpuz

Faculty

FIGURE 4 Given Requirements:

- $I_{\text{max}} \approx 750 \text{ mA}$
- $V_{\text{ripple}} = 0.10V_p$
- Maximum center-tap $V_m = 12 \times 2 = 24V$
- Using LM317A voltage regulator

Parameters	Computed
V_m	24 V (Given)
V_{mp}	33.94 V
V_{k1}	0.7 V
V_{k2}	0.7 V
V_{k3}	0.7 V
V_{k4}	0.7 V
V_{dc}	20.70 V
V_{ripple}	0.10 V (Given)
V_{in} (LM317)	3V-40V , so $V_{dc} = 20.70V$ is check
R_L (ideal)	27.6 Ω
R_L (actual)	45.25 Ω
PD R_L (ideal)	15.525 W
PD R_L (actual)	25.455 w
V_{R1}	1.25v
I_{R1}	5.21 mA
V_{R2min}	0.00 V
I_{R2min}	0.00 A
V_{R2max}	16.446 V

IR _{2max}	5.21mA
C1	62,500 μ F
C2	1 μ F
V _{omin} (pureDC)	1.25 V
V _{omax} (pureDC)	17.70 V
I _{omin} (pureDC)	45.30 mA
I _{omax} (pureDC)	0.75 A or 750mA
FI	60 Hz
FO	120 Hz

Parameters	Solutions and Justifications
V _m	24 V (Given)
V _{mp}	$V_{mp} = V_m \sqrt{2} = 24\sqrt{2} = \mathbf{33.94\ V}$
V _{k1}	0.7 V (diode voltage drop) This value is dependent on the diode's material, typically 0.6-0.7V for silicon diodes
V _{k2}	0.7 V (diode voltage drop) This value is dependent on the diode's material, typically 0.6-0.7V for silicon diodes
V _{k3}	0.7 V (diode voltage drop) This value is dependent on the diode's material, typically 0.6-0.7V for silicon diodes



V _{k4}	0.7 V (diode voltage drop) This value is dependent on the diode's material, typically 0.6-0.7V for silicon diodes
V _{dc}	$V_{dc} = 0.636(V_{mp} - 2V_k) = 0.636 [33.94 - (2 \times 0.7)] = \mathbf{20.70\ V}$
V _{ripple}	0.10 V (Given)
V _{in} (LM317)	According to datasheet: 3V-40V , so V_{dc} = 20.70V is check
R _L (ideal)	$R_L = V_{dc} / I_o = 20.70 / 0.750 = \mathbf{27.6\ \Omega}$
R _L (actual)	$R_L = V_{mp} / I_o = 33.94 / 0.750 = \mathbf{45.25\ \Omega}$
P _D R _L (ideal)	$P_D = I V_{dc} = (0.750 \times 20.70) = \mathbf{15.525\ W}$
P _D R _L (actual)	$P_D = I V_{mp} = (0.750 \times 33.94) = \mathbf{25.455\ w}$
V _{R1}	LM317A has a built-in reference voltage (V _{ref}) of about 1.25 V between its output pin and adjust pin.
I _{R1}	$V_{ref} / R_1 = 1.25v / 240\ ohms = 0.0052083333$ $= \mathbf{5.21\ mA}$
V _{R2min}	Minimum LM317 output = V _{ref} ($\approx 1.25\ V$). If output set to V _{ref} , across R ₂ there is 0 V so R ₂ current is 0 (ignoring I _{adj}).

IR2min	Practically zero; tiny Iadj exists but negligible here
VR2max	VR2max= Vomax - Vref = 17.70–1.25= 16.45V
IR2max	VR2max / R2 = 16.45V / 3157.66 ohms = 0.00520833 A = 5.21 mA
C1	$C1 = I * T / \Delta V$ <ul style="list-style-type: none"> • Compute $T = 1/120 = 0.008333333333 \text{ s}$ • $T = 1/120 = 0.008333333333 \text{ s}$ • $I * T = 0.750 \text{ A} \times 0.008333333333 \text{ s}$ = 0.00625 • Divide by ΔV (0.10 V): $C = 0.00625 \div 0.10 = 0.0625 \text{ F}$ • Convert to μF: $0.0625 \text{ F} = 62,500 \mu\text{F}$ • Result: $C1 = \mathbf{62,500 \mu F}$
C2	<p>LM317 datasheet and module recommend a small bypass on the adjust or output (typical values 1 μF for adjust bypass to improve ripple rejection). Also an input bypass $\sim 0.1 \mu\text{F}$ near regulator recommended.</p> <ul style="list-style-type: none"> • Result (practical): $C2 = \mathbf{1 \mu F}$ (adjust/output bypass) and 0.1–0.33 μF (input bypass) as per datasheet practice.
Vomin (pureDC)	LM317 minimum output is Vref ($\approx 1.25 \text{ V}$) when $R2 = 0$.

Vomax (pureDC)	<p>LM317 requires headroom; approximate $V_{omax} \approx V_{dc} - V_{dropout}$. Using assumed dropout ≈ 3.0 V</p> <ul style="list-style-type: none"> • $V_{dc} = 20.70$ V • $V_{omax} = 20.70V - 3.0v = 17.696$ V • Rounded result: $V_{omax} \approx \mathbf{17.70V}$
Iomin (pureDC)	<p>V_{omin} / R_L (ideal) = $1.25v / 27.60$ ohms = 0.045289 A</p> <p>= 45.30 mA</p>
Iomax (pureDC)	0.750 A or 750mA – given design or requirement
FI	60 Hz - standard frequency used (here in Philippines)
FO	$2 \times FI = \mathbf{120 Hz}$

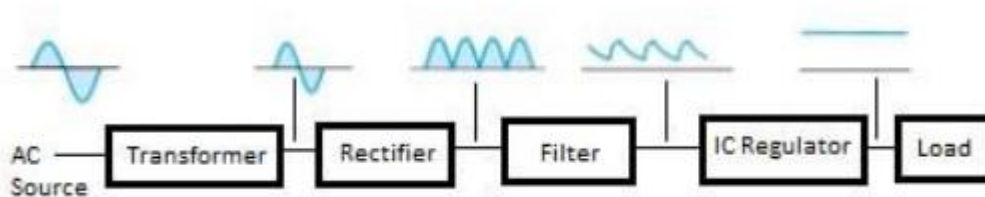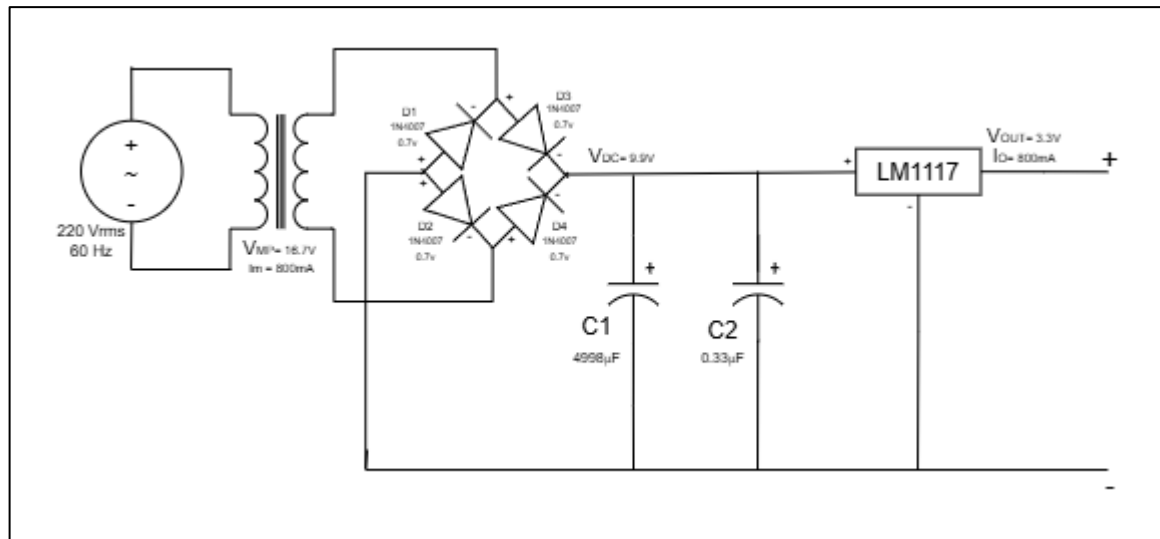2. In reference to your previous proposed IPO/block model in Modules 1 and 2, design the appropriate power supply system. Present the following requirements:

- Schematic circuit design
- Computational solution/s for each electronic component, including justification if necessary



A Direct Current (DC) voltage regulator takes in an analog voltage signal and converts it into a stable, regulated, DC voltage. This is achieved through various components: The transformer that steps down (or steps up depending on the engineer) a given Alternating Current (AC) voltage to a much lower voltage peak. The rectifier that converts the stepped down voltage into pulsating DC. A Filter which is usually in the form of a capacitor is then utilized to try and smoothen out the rectified DC signal. Lastly, an IC Regulator that would stabilize the filtered pulsating DC into a pure and stable DC output. For this circuit, a step down transformer with a 12 V_{AC} secondary winding would be utilized. The transformer type to be used is a center—tapped, (6-0-6) transformer. The IC Regulator to be utilized is Texas Instruments' LM1117, 800mA that would output 3.3v. From the

revised proposed IPO Model with respect to the tasks from Module 1 and 2, the load would be Espressif System's ESP32-WROOM-32UE.

3.3V Regulated DC Fixed Power Supply	
Step 1: Transformer -> Rectifier	
Transformer Peak Voltage	<p>Peak Voltage Formula:</p> $V_{MP} = V_m \sqrt{2}$ <p>Solution:</p> $V_{MP} = 12.0 \times 1.41421356$ $V_{MP} = 16.97V$
Calculate V_{DC}	<p>V_{DC} Formula:</p> $V_{DC} = 0.636 \times (V_{mp} - 2V_k)$ <p>Solution:</p> $V_{DC} = 0.636 \times (16.97 - 1.4)$ $V_{DC} = 9.9V$ <p>Justification:</p> <p>$V_{DC} = 9.9V$ gives enough headroom for the LM1117 to regulate voltage to 3.3v. According to the Texas Instrument LM1117, 800mA data sheet, the dropout voltage is 1.2v at $V_{TYPICAL}$ and 1.3v at V_{MAX}.</p>
Transformer Current Rating	Transformer Current = 800mA

	<p>Justification:</p> <p>According to the Espressif Systems ESP32-WROOM-32UE data sheet, the recommended current delivered by an external power supply to the ESP32 module is 500mA at minimum with the typical and maximum to be desired by the engineer. Since this is the case, an additional 300mA increase would be ample headroom in the case of sudden power draws. Furthermore, the IC to be utilized is rated at 800mA.</p>
Step 2: Bridge Rectifier	
Bridge Rectifier Details	<p>The Rectifier would host a bridge-type system composing of 4 silicon diodes with 0.7v of voltage drop each. The silicon diode model to be utilized is the 1N4007.</p> <p>Justification:</p> <p>The aforementioned diode model would be utilized since the diode can survive reverse voltage of up to 1000v.</p>
Step 3: Filter Capacitor	
Calculate the Capacitor Value (Capacitance)	<p>Filter Capacitance Formula:</p> $C = (IT)/V$ <p>Where in:</p> <p>T= 8.33ms (Full Wave)</p> <p>V= $0.5V_{pp}$</p>

	<p>Solution:</p> $C = (0.3 \times 0.00833) / 0.5$ $C = 0.004998\text{F}$ $C = 4998 \mu\text{F}$ <p>Justification:</p> <p>A 25V electrolytic capacitor for safety as the filter should be higher or equal to the V_{DC}.</p>
Step 4: Input Decoupling After Filter Capacitor	
<p>0.33μF Film/Ceramic Capacitor</p>	<p>Justification:</p> <p>This functions as a small high frequency component that by passes the ground to remove HF spikes that large electrolytics miss. The voltage rating for this capacitor is also equal to C3 which is 25V electrolytic.</p>
Step 5: IC Voltage Regulator	
<p>LM1117 Details,</p>	<p>According to Texas Instruments' LM1117, 800mA Data Sheet, the LM1117 is a voltage regulator that steps down and regulates a pulsating DC voltage into a stable 3.3V. It's input voltage max is 20v and a dropout voltage of 1.2V at $V_{TYPICAL}$ and 1.3v at V_{MAX}. Furthermore, it is rated at 800mA.</p>

	<p>Justification:</p> <p>Since the load requires a voltage input of 3.3v and also has a current draw of 800mA, the LM1117 serves as the best voltage regulator component that fits the requirements needed to properly run the load.</p>
Step 6: Load	
Espressif Systems ESP32-WROOM-32UE	<p>From the revised proposed IPO Model with respect to the tasks from Module 1 and 2, the load would be Espressif System’s ESP32-WROOM-32UE. This microcontroller would be utilized for the proposed Room-Level Fire Prediction System that would utilized various components for room fire prediction. According to the Espressif System’s ESP32-WROOM-32UE Data Sheet, the recommended operating conditions of the microcontroller are the following:</p> <p>$V_{MIN}= 3V$</p> <p>$V_{TYPICAL}= 3.3V$</p> <p>$V_{MAX}= 3.6V$</p> <p>$I_{MIN}= 500mA$</p> <p>From these operating conditions alone, the following computations and components utilized for the 3.3v Regulated Power Supply are justified. With this, the 3.3V Regulated DC Fixed Power Supply has the following output.</p> <p>$V_o= 3.3V$</p>

	$I_o = 800mA$
--	---------------

References:

- Espressif Systems. (2021). *ESP32-D0WD-V3 Datasheet*. ALLDATASHEET.COM. <https://www.alldatasheet.com/datasheet-pdf/pdf/1242996/ESPRESSIF/ESP32-D0WD-V3.html>
- Texas Instruments. (2023, January). TI.com. https://www.ti.com/lit/ds/symlink/lm1117.pdf?ts=1759082277413&ref_url=https%253A%252F%252Fwww.mouser.in%252F

3. Specify the percentage contribution of each group member (100% total). Each member should sign to confirm the breakdown of contribution.


Contributions of each group member:

ARENAS, JOSEPH	20%
ESTRADA, CYRUS.....	20%
GUTIERREZ, GEO KENTZER.....	20%
PACIS, LIAN GIL	20%
RECAÑA, JORDAN	20%
TOTAL	100%

Signature of each group member:

A handwritten signature in black ink, featuring a large, stylized 'J' and 'A' that are connected and flow into a series of loops and a final horizontal stroke.


ARENAS, JOSEPH

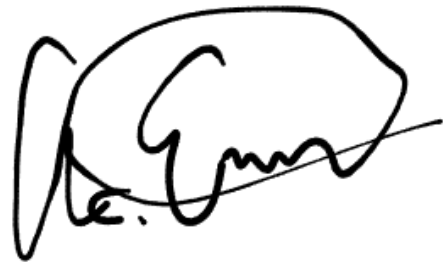A handwritten signature in black ink, starting with a large, bold 'E' and 'C' that are connected, followed by a series of loops and a final horizontal stroke.

ESTRADA, CYRUZ

A handwritten signature in black ink, featuring a large, stylized 'G' and 'K' that are connected, followed by a series of loops and a final horizontal stroke.

GUTIERREZ, GEO KENTZER

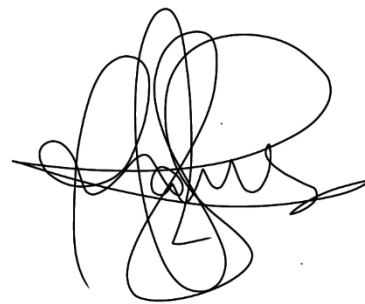A handwritten signature in black ink, featuring a large, stylized 'L' and 'G' that are connected, followed by a series of loops and a final horizontal stroke.

PACIS, LIAN GIL

A handwritten signature in black ink, featuring a large, stylized 'J' and 'R' that are connected, followed by a series of loops and a final horizontal stroke.

RECAÑA, JORDAN