



Name: \_\_\_\_\_  
Course/Year/Section: \_\_\_\_\_  
Date Started: \_\_\_\_\_ Date Submitted: \_\_\_\_\_  
Assessed by: \_\_\_\_\_ Rating: \_\_\_\_\_

## SUPPORT CIRCUIT DESIGN 1

### Module 3

#### I. OBJECTIVES

At the end of the lesson, the students are expected to:


1. Learn the basic electronic circuits used to support microcomputer systems, such as a regulated power supply.
2. Appreciate the importance of certain electronic circuits to optimize the performance of various microcomputer applications.
3. Design a regulated power supply based on specific parameters or requirements.

#### II. GENERAL INFORMATION

1. **SUPPORT CIRCUIT DESIGNS** – complimentary electro-mechanical circuits that are designed to help microcomputers systems optimize their performance. In the context of this module, the focus will be on the design of a regulated power supply.
2. **BASIC OHM'S LAW FORMULAS:**
  - a.  $E = IR$  = electromotive force (voltage, measured in volts or v) is the product of current (intensity, measured in A) and resistance (measured in ohms or  $\Omega$ )
  - b.  $I = E/R$  = current is the quotient of voltage and resistance
  - c.  $R = E/I$  = resistance is the quotient of voltage and current.
  - d.  $P = EI$  = power is the product of voltage and current.
  - e.  $P = I^2R$  = power is the product squared current and resistance.
  - f.  $P = E^2/R$  = power is the quotient of squared voltage over and resistance.
3. **REGULATED POWER SUPPLY** – a direct current (DC) power supply used to provide stable, regulated power source to MCU and its system peripherals.

**Figure 1**


*DC Regulated Power Supply Design*

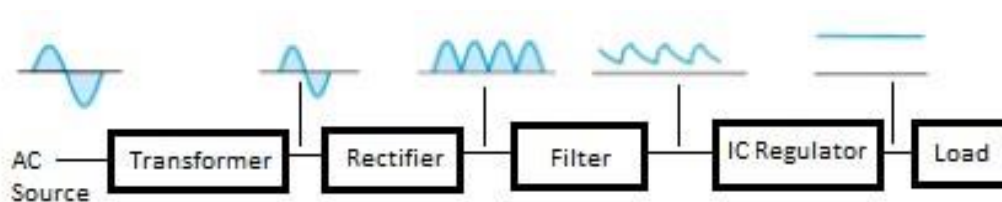



**Figure 2**

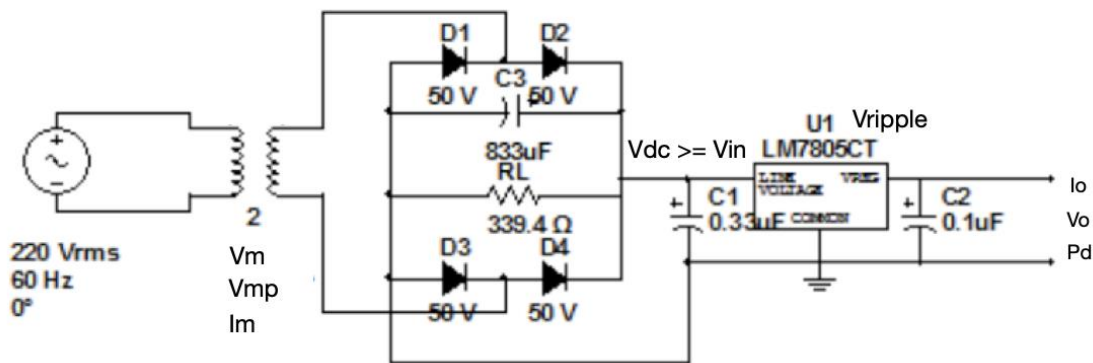*DC Regulated Power Supply Sample Schematic Diagram*



#### 4. DESIGN CONSIDERATIONS

- The load ( $R_L$ ) is the output component. Parameters  $I_o$  and  $V_o$  or  $V_{dc}$  requirements should be considered first.  $R_L = V_o/I_o$  or  $R_L = V_{dc}/I_o$ .
- The power dissipation ( $P_D > I_o V_o$ ) of the  $R_L$  to be used in laboratory should be greater than the computed value.
- Check the  $V_{mp}$  = voltage rating of the secondary winding of the transformer; it should ably meet the required range at the line voltage ( $V_{in}$ ) of the regulator IC – refer to the datasheet.
- Check the  $I_m$  = maximum current rating of the transformer, which should able support the required current output of the power supply design. If  $I_O$  is stated as maximum, the designer can choose the desired  $I_o$  that fits within the range.
- Compute for the peak voltage rating of the  $V_m$  by using the formula:  $V^{mp} = V_m \sqrt{2}$
- Using a general-purpose diode for the bridge-type rectifier circuit, the  $V_k = 0.7V$  (Si).
- The equivalent DC voltage of a power supply design is computed as  $V_{dc} = 0.636 (V_{mp} - 2V_k)$  for full wave;  $V_{dc} = 0.318 (V_{mp} - V_k)$  for half-wave.
- To compute for the Filter Capacitor (FC), consider the formula:  $C = IT/V$ , where  $C$  is the capacitance (usually in  $\mu F$ ),  $I$  is the current that flows into the capacitor (usually in mA),  $T$  (full wave = 8.33 ms; half wave = 16.64 ms); and  $V$  is the  $V_{ripple}$  ( $V_{pp}/2 = 0.5/2 = 0.25V_p$ ).
- Ripple is the fluctuating DC filtered out from the rectifier circuit and can be expressed as  $V_{pp}/2$  or  $V_p$  value which should be ideally  $\leq 0.5V_{pp}$ .



- It is computed by the formula:  $V_{\text{ripple}} = V_{\text{dc}} (1 - e^{-T/RLC})$ ; where  $R_L$  is the load resistance;  $T$  is the time element of the design; and  $C$  is the assumed capacitor value.
- Note that  $V_o$  can be  $V_{\text{dc}}$  (use  $R_L = V_{\text{dc}}/I_o$ ) or  $V_{\text{mp}}$  ( $R_L = V_{\text{mp}}/I_o$ ).
- Note that the formulas  $C=IT/V$  and  $V_{\text{ripple}} = \Delta V = V_{\text{max}} - V_{\text{min}} \approx V_{\text{dc}} (1 - e^{-T/RLC})$  may not be exactly equal due to some tolerance considerations such as noise, etc., but can be used interchangeably depending on the choice of the designer.
- $C$  is inversely proportional to  $V$ , hence, the higher the  $C$  value, the lower the voltage ripple.
- The output frequency for half wave is equal to the input ( $f_i = f_o$ ), which is 60Hz for 220VAC; while for full wave,  $f_o = 2f_i$ , which is  $2 \times 60 = 120\text{Hz}$ .
- **For Fixed Regulator IC**
  - a. Check for pin configuration of the regulator IC's  $V_{\text{in}}$ , G (ground), and  $V_o$  terminals.
  - b. Ensure that the  $V_{\text{mp}} \geq V_{\text{in}}$  by referring on the datasheet of the regulator IC.
  - c. Follow the recommended optimization circuit as stated on the datasheet of the regulator IC such as the  $C_1$  and  $C_2$  components and others.
  - d. The output of the regulator IC indicates the  $V_{\text{min}} \mid V_{\text{typical}} \mid V_{\text{max}}$  with equivalent test conditions  $I_{\text{min}} \mid I_{\text{typical}} \mid I_{\text{max}}$
- **For Adjustable Regulator IC**
  - a. Check for pin configuration of the regulator IC's  $V_{\text{in}}$ ,  $V_{\text{Adj}}$  (Adjust), and  $V_o$  terminals.
  - b. Ensure that the  $V_{\text{mp}} \geq V_{\text{in}}$  by referring on the datasheet of the regulator IC.
  - c. Follow the recommended optimization circuit as stated on the datasheet of the regulator IC such as the  $C_1, C_2, R_1, R_2$  and others components.
  - d. Output capacitors ( $C_2$ ) are usually in the range of 1  $\mu\text{F}$  to 1000  $\mu\text{F}$ , unless stated.
  - e. The output voltage ( $V_o$ ) of the regulator IC indicates the  $V_{\text{ref}}$  or  $V_{\text{min}}$  ( $1.25V_{\text{typ}} \mid V_{\text{max}} \mid I_{R2\text{max}}$  (100uA) also known as Adjustment Pin Current. The average output voltage of the regulator IC is computed as  $V_o = V_{\text{ref}}(1 + R_2/R_1) + (I_{\text{adj}} * R_2)$
  - f. Note that for negative and positive regulator circuits, same formulas can be used.
- **For Adaptor/ Charger**
  - a. The  $V_o$  and  $I_o$  of the adaptor substitute the  $V_m$  and  $I_m$  parameters of the transformer.




- b. Additional half-wave or full-wave rectifier circuits can be used and follow the same design considerations as using the conventional transformer method.

### III. SAMPLE DESIGN

Design a DC regulated, bridge type, full wave, power supply with  $I_o \approx 50\text{mA}$ ,  $V_o \approx 5\text{V}$ ,  $V_m = 12\text{-}0\text{-}12\text{V}$  (Center-tap, just use  $V_m = 12\text{V}$ ),  $I_m = 750\text{mA}$ ,  $V_k = 0.7\text{V}$ , and  $V_{\text{ripple}} = 0.5\text{V}_{\text{pp}}$ .

**Figure 3**  
*Power Supply Design 1*

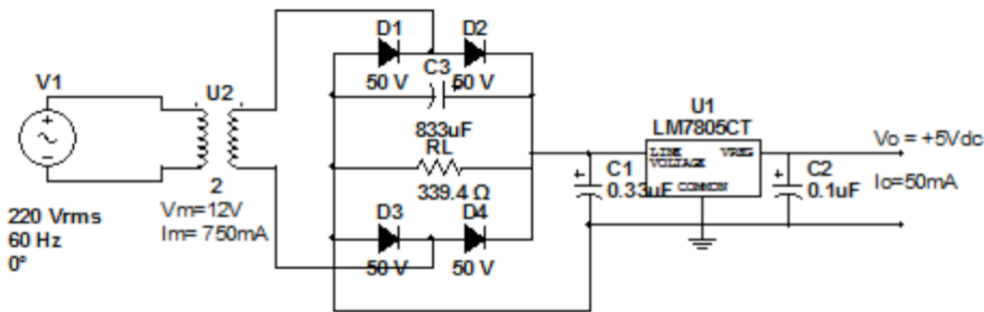


- $V_{\text{mp}} = V_m \sqrt{2} = 12\sqrt{2} = 16.97\text{V}$
- $V_{\text{dc}} = 0.636(V_{\text{mp}} - 2V_k) = 0.636[16.97 - (2 \cdot 0.7)] = 9.90\text{V}$  (full wave)
- $C = IT/V = (50^{-3} \cdot 8.33^{-3}) / 0.5V_{\text{pp}} = 833\mu\text{F}$
- $R_L = V_{\text{dc}} / I_o = 9.90 / 50^{-3} = 198\Omega$  with  $P_D = IV = 50^{-3} \cdot 9.90 = 0.495\text{W}$  (ideal)
- $R_L = V_{\text{mp}} / I_o = 16.97 / 50^{-3} = 339.4\Omega$  with  $P_D = IV = 50^{-3} \cdot 16.97 = 0.849\text{W}$  (actual)
- $V_{\text{ripple}} = V_{\text{dc}}(1 - e^{-T/R_L C}) = 9.90(1 - e^{-0.00833/[198 \cdot 0.000833]}) = 0.5V_{\text{pp}}$
- According to the LM7805 datasheet,  $V_{\text{in}} = 7\text{V}-20\text{V}$ , hence,  $V_{\text{dc}} = 9.90\text{V}$  is check.
- According to the LM7805 datasheet, optimization components should be  $C_1 = 0.33\mu\text{F}$  and  $C_2 = 0.1\mu\text{F}$ .
- According to the LM7805 datasheet,  $I_m = 750\text{mA}$ ,  $I_o = 5\text{mA}-1\text{A}$ , hence,  $I_o = 50\text{mA}$  is check.
- According to the LM7805 datasheet,  $V_{\text{min}} = 4.8\text{V}$ ,  $V_{\text{ave}} = 5\text{V}$  and  $V_{\text{max}} = 5.2\text{V}$ ,  $V_o = 5\text{V}$  is check.



#### IV. CHECKPOINT

In reference to the above concepts, design a regulated **adjustable power supply** with  $I_{\text{omax}} \approx 750 \text{ mA}$ ,  $V_{\text{ripple}} = 0.10V_p$ , and maximize the center-tap  $V_m = 12 \times 2 = 24\text{V}$ . Use LM317A, refer to its datasheet, and complete the table below. Show solutions.

**Figure 4**  
*Power Supply Design 2*

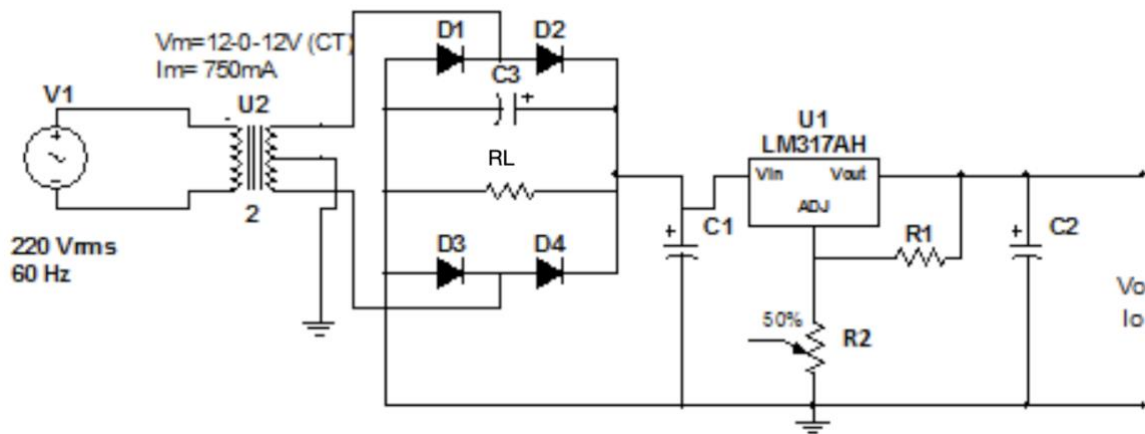

Parameter	Computed
$V_m$	
$V_{mp}$	
$V_{k1}$	
$V_{k2}$	
$V_{k3}$	
$V_{k4}$	
$V_{dc}$	
$V_{\text{ripple}}$	
$V_{\text{in}} \text{ (LM317)}$	
$R_L \text{ (ideal)}$	
$R_L \text{ (actual)}$	
$P_{D \text{ } R_L} \text{ (ideal)}$	
$P_{D \text{ } R_L} \text{ (actual)}$	
$V_{R1}$	
$I_{R1}$	
$V_{R2\text{min}}$	
$I_{R2\text{min}}$	
$V_{R2\text{max}}$	



$I_{R2max}$	
$C_1$	
$C_2$	
$V_{omin} \text{ (pureDC)}$	
$V_{omax} \text{ (pureDC)}$	
$I_{omin} \text{ (pureDC)}$	
$I_{omax} \text{ (pureDC)}$	
$F_I$	
$F_O$	

2. In reference to your previous proposed IPO/block model in Modules 1 and 2, design the appropriate power supply system. Present the following requirements:

- Schematic circuit design
- Computational solution/s for each electronic component, including justification if necessary.