

---

## *INTRODUCTION TO HDL*

---

TECHNOLOGICAL UNIVERSITY OF THE PHILIPPINES

Ayala Blvd. cor San Marcelino St. Ermita, Manila

### CPET7L Hands On Activity 2

**CPET – 2A**

Tuesday 4:00PM to 7:00 PM

Submitted By:

Pacis, Lian Gil  
Recaña, Jordan  
Gutierrez, Geo Kenzter  
Arenas, Joseph  
Estrada, Adriene Cyruz

Submitted To:

Engr. AIMEE G. ACOBA  
CPE Faculty

# INTRODUCTION TO HDL

Questions:

## Task Assessment:


**Part 1: Programming Exercises: Create a Dataflow Modeling Verilog HDL program for the following statement:**

1. Listed down the Basic codes in Verilog program
  - a. 2 input - OR gate
  - b. 2 input - NAND gate
  - c. 3 input - NOR gate
  - d. 3 input - XOR gate
  - e. 3 input - XNOR gate

## Part 2: Full Adder

1. Full Adder is the adder which adds three inputs and produces two outputs. The first two inputs are A and B and the third input is an input carry as Carry in. The output carry is designated as Carry out and the normal output is designated as S which is SUM.
2.  $S = A \oplus B \oplus \text{Cin}$        $C = AB + \text{Cin} (A \oplus B)$

A	B	Carry in	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Answers:

Part 1 A:

```
module ORGATE(a, b, x);
    input a, b;
    output x;
    assign x = a | b;
endmodule

module testbench;
    reg a, b;
    wire x;

    // Instantiate the ORGATE module
```

```
ORGATE U1 (a, b, x);
```

```
initial begin
```

```
    $display ("a b | x");
```

```
    a = 0;
```

```
    b = 0;
```

```
    #4 $finish;
```

```
end
```

```
always #2 a = ~a;
```

```
always #1 b = ~b;
```

```
initial begin
```


```
    $monitor ("%b %b | %b", a, b, x);
```

```
end
```

```
endmodule
```

# INTRODUCTION TO HDL

## OUTPUT PART 1A:

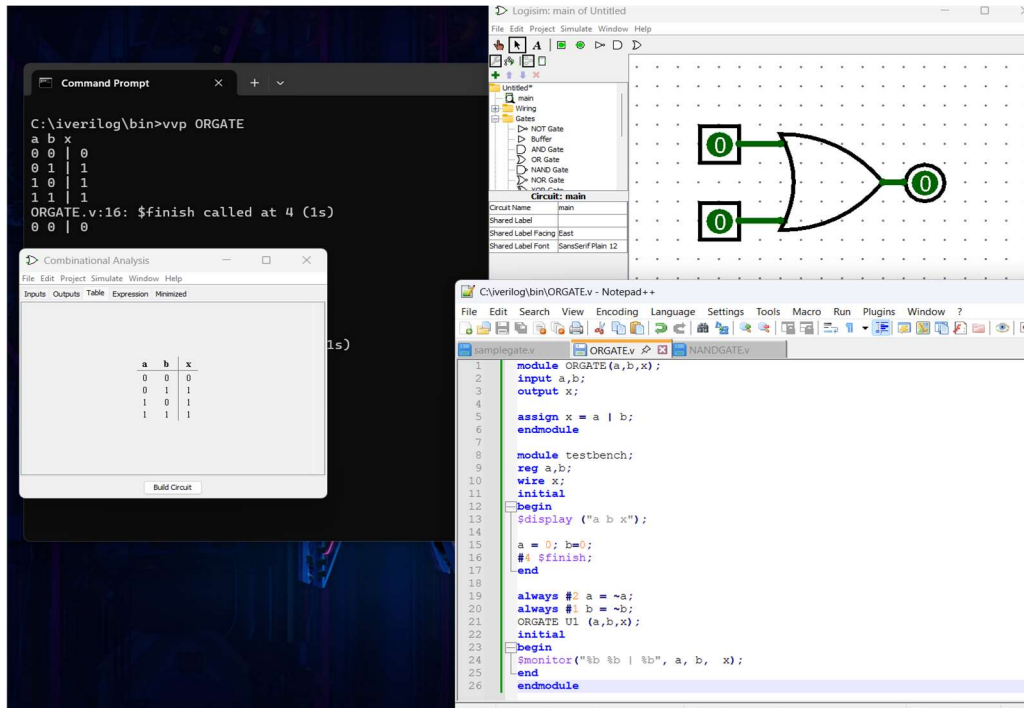

## Part 1 B:

```
module NANDGATE(a,b,x);
input a,b;
output x;
assign x = ~(a & b);
endmodule


module testbench;
reg a,b;
wire x;
initial
begin
  $display ("a b x");
  a = 0;
```

```
b = 0;
  #4 $finish;
end

always #2 a = ~a;
always #1 b = ~b;
NANDGATE U1 (a,b,x);
initial
begin
  $monitor ("%b %b | %b", a, b, x);
end
endmodule
```

# INTRODUCTION TO HDL

## OUTPUT PART 1B:

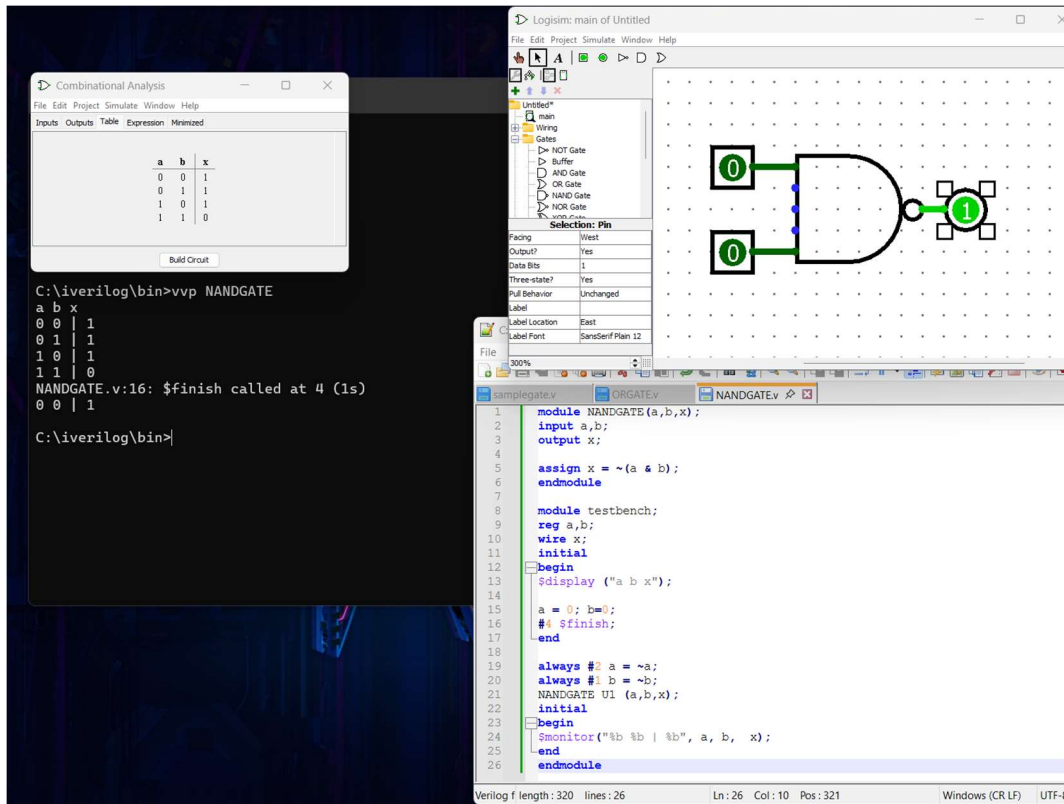

## PART 1 C:

```
module norgate_3in(a, b, c, x);

input a, b, c;

output x;

assign x = ~(a | b | c);

endmodule

module test_bench;

reg a, b, c;

wire x;

initial

begin

  $display ("a b c | x");

  a = 0;
```

```
b = 0;

c = 0;

#8 $finish;

end

always #4 a = ~a;

always #2 b = ~b;

always #1 c = ~c;

norgate_3in U1 (a, b, c, x);


initial

  $monitor ("%b %b %b | %b", a, b, c, x);

endmodule
```

# INTRODUCTION TO HDL

## OUTPUT PART 1C:

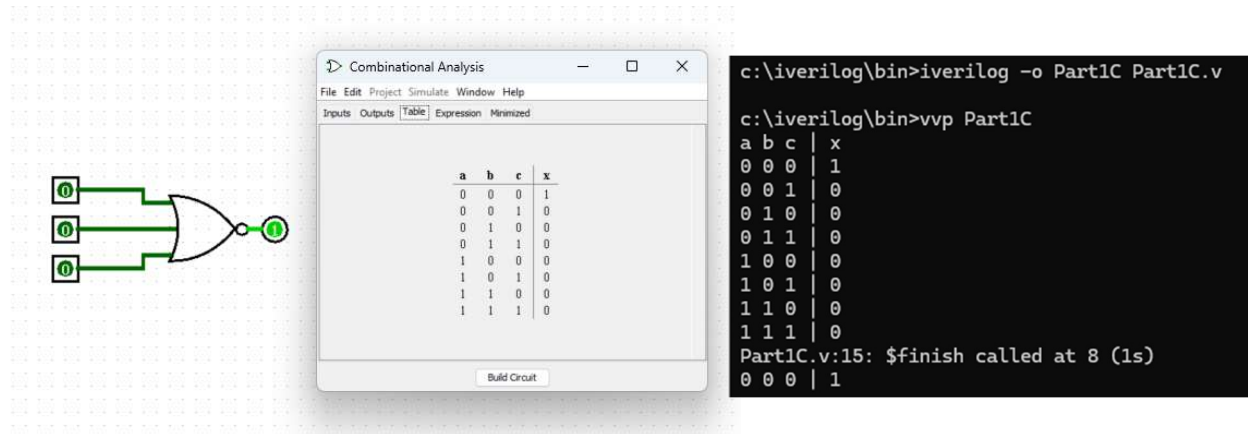

The screenshot displays three components related to a combinational logic circuit simulation:

- Logic Diagram:** A circuit with three input variables (a, b, c) connected to a 3-input OR gate, which produces the output x.
- Truth Table:** A table showing the output x for all possible combinations of inputs a, b, and c.
- Terminal Window:** A window showing the command-line execution of IVerilog, including the compilation of Part1C.v and the simulation results.

a	b	c	x
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

```
c:\iverilog\bin>iverilog -o Part1C Part1C.v
c:\iverilog\bin>vvp Part1C
a b c | x
0 0 0 | 1
0 0 1 | 0
0 1 0 | 0
0 1 1 | 0
1 0 0 | 0
1 0 1 | 0
1 1 0 | 0
1 1 1 | 0
Part1C.v:15: $finish called at 8 (1s)
0 0 0 | 1
```

## PART 1 D:


```
module gald (a, b, c, x);
input a, b, c;
output x;
assign x = (a ^ b ^ c);
endmodule

module test_bench;
reg a, b, c;
wire x;
initial
begin
    $display ("A B C | X");
    a = 0;
    b = 0;
    c = 0;
    #8 $finish;
end
always #4 a = ~a;
always #2 b = ~b;
```

```
always #1 c = ~c;
gald U1 (a, b, c, x);
initial
    $monitor ("%b %b %b | %b", a, b, c, x);
endmodule
```

# INTRODUCTION TO HDL

## OUTPUT PART 1D:

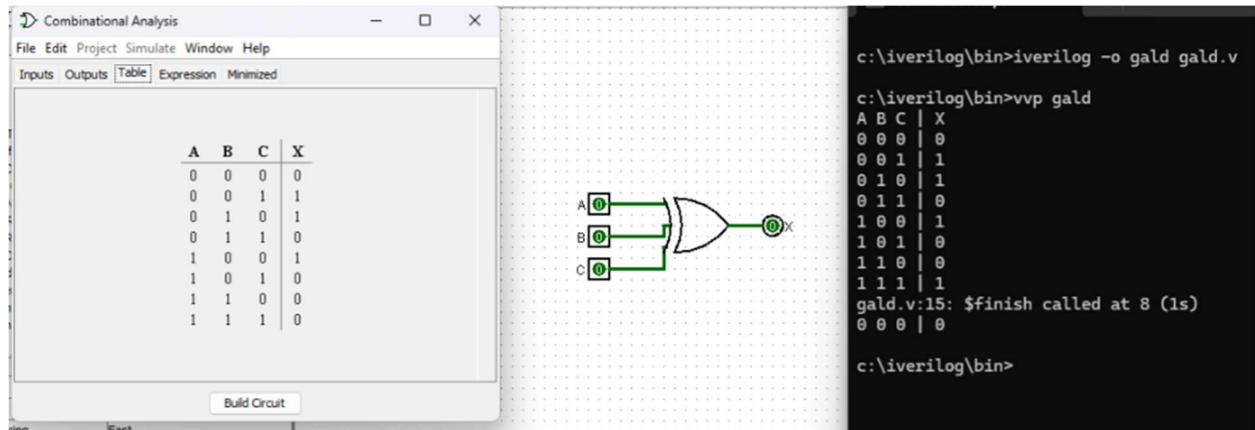

The screenshot displays the 'Combinational Analysis' window with three panes:

- Table:** A truth table for a 3-input OR gate with inputs A, B, and C, and output X.
- Diagram:** A logic diagram showing three inputs A, B, and C connected to a 3-input OR gate, with the output labeled X.
- Terminal:** A command prompt showing the execution of iverilog and vvp commands, followed by the simulation output.

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

```
c:\iverilog\bin>iverilog -o gald gald.v
c:\iverilog\bin>vvp gald
A B C | X
0 0 0 | 0
0 0 1 | 1
0 1 0 | 1
0 1 1 | 1
1 0 0 | 1
1 0 1 | 1
1 1 0 | 1
1 1 1 | 1
gald.v:15: $finish called at 8 (1s)
0 0 0 | 0
c:\iverilog\bin>
```

## PART 1 E:

```
module samplegate (a, b, c, x);
    input a, b, c;
    output x;
    assign x = (~a & ~b & ~c) | (b & c) | (a & c) | (a
    & b);
endmodule

module test_bench;
    reg a, b, c;
    wire x;

    initial
    begin
        $display ("t a b c | x");

        a = 0;
        b = 0;
        c = 0;

        #8 $finish;
    end
end
```

```
always #4 a = ~a;
always #2 b = ~b;
always #1 c = ~c;

samplegate U1 (a, b, c, x);


initial

    $monitor ("%g %b %b %b %b", $time, a, b, c,
    x);

endmodule
```

# INTRODUCTION TO HDL

## OUTPUT PART 1E:

 

a	b	c	x
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

```
c:\iverilog\bin>iverilog -o samplegate samplegate.v
c:\iverilog\bin>vvp samplegate
t a b c | x
0 0 0 0 | 1
1 0 0 1 | 0
2 0 1 0 | 0
3 0 1 1 | 1
4 1 0 0 0 | 0
5 1 0 1 | 1
6 1 1 0 | 1
7 1 1 1 | 1
samplegate.v:15: $finish called at 8 (1s)
8 0 0 0 | 1
c:\iverilog\bin>
```

## PART 2:

```
module task2 (a,b,cin,sum,cout);
input a,b,cin; output sum,cout;

assign sum = a ^ b ^ cin; assign cout = (a & b) |
cin & (a ^ b);

endmodule

module TestBench;
reg a,b,cin; wire sum,cout;

initial
begin
    $display("A B Cin Sum Cout");

    a = 1'b0;
    b = 1'b0;
```

```
    cin = 1'b0;
    #8 $finish;

end

always #4 a = ~a;
always #2 b = ~b;
always #1 cin = ~cin;

task2 U1(a,b,cin,sum,cout);

initial

$monitor("%b %b %b %b %b",
"a,b,cin,sum,cout");


endmodule
```

## OUTPUT:

$$2. \quad S = A \oplus B \oplus \text{Cin}$$

$$C = AB + \text{Cin} (A \oplus B)$$

A	B	Carry in	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

```
C:\iverilog\bin>iverilog -o task2 task2.v
C:\iverilog\bin>vvp task2
A B Cin Sum Cout
0 0 0 0 0
0 0 1 1 0
0 1 0 1 0
0 1 1 0 1
1 0 0 1 0
1 0 1 0 1
1 1 0 0 1
1 1 1 1 1
task2.v:14: $finish called at 8 (1s)
```